
# GTU Department of Computer Engineering CSE 331/503 - Fall 2022 Final Project

Emirkan Burak Yılmaz 1901042659

#### 1. mips\_single\_cycle\_16

 

The processor consists of control unit and datapath. The control unit produces the required signals that datapath needs. There are general signals like reg\_dst reg\_write and instructions specific signals like jump, beq. Supported instructions and some instruction examples are given below.

R-type: add, sub, slt, and, or, sll, srl, mult I-type: addi, lw, sw, li, beq, bne, slti, andi, ori


J-type: j, jr, jal

INSTR R-TYPE	func(hex)	Opcode	rs	rt	rd	shamt	func	
add \$r1, \$r2, \$r3	20	000000	0010	0011	0001	0000	100000	0000
and \$r1, \$r4, \$r5	24	000000	0100	0101	0001	0000	100100	0000
sub \$r1, \$r2, \$3	22	000000	0010	0011	0001	0000	100010	0000
or \$r1, \$r4, \$r5	25	000000	0100	0101	0001	0000	100101	0000

INSTR I-TYPE	opcode (hex)	opcode	rs	rt	lmm16	
addi \$r1, \$r2, 15	08	001000	0010	0001	0000 0000 0000 1111	00
slti \$r1, \$r6, 26	0a	001010	0110	0001	0000 0000 0001 1010	00
andi \$r1, \$r5, 1023	0c	001100	0101	0001	0000 0011 1111 1111	00
li \$r2, 100	07	000111	0000	0010	0000 0000 0110 0100	00
lw \$r1, \$r0, 4	23	100011	0000	0001	0000 0000 0000 0100	00
ori \$r5, \$r1, 0	0d	001101	0001	0101	0000 0000 0000 0000	00

INSTR J-TYPE	opcode (hex)	opcode	addr	
j 2	02	000010	00 0000 0010	0000 0000 0000 0000


# 2. control\_unit

 


Control unit takes the opcode and the function part of the instruction and produces control signals. The following shows the signals and their meaning.

Signal	Meaning	
reg_dst	Selects rt or rd register for write register address	
beq	beq instruction	
bne	bne instruction	
jump	j instruction	
jumpr	jr instruction	
jumpal	jal instruction	
loadi	li instruction	
reg_write	Enables register write port	
alu_ctr	Selects ALU operation	
alu_src	Select immediate or value from rt register	
mem_read	Enables data memory read	
mem_write	Enables data memory write	
mem_to_reg	Select the data comes from memory or ALU result	

#### 3. datapath

 

 
MIPS follows Harvard architecture and uses separate memories for instruction and data. In this design instructions are kept in a ROM which has capacity of  $2^{10}$  instruction (32-bit instruction) and data are kept in a RAM which has capacity of  $2^{16}$  words (16-bit word). For these two types of memory data\_mem and instr\_mem modules are created with Quartus MegaWizard.



For the registers register\_file module created, and it contains registers module which created with Quartus MegaWizard. Register file has 16 registers inside and it has 2 ports. Reading and writing operations are done in half cycle. For accomplish this half cycle execution, fast\_clock is used. It has double frequency when we compared to main clock.

Datapath also contains ALU for executing the instructions by doing arithmetic and logical operations.

## 4. alu\_16

 


ALU is implemented with structural verilog and it supports 8 different operations. Basically, all the operations are calculated, and the result is selected with control signal alu\_ctr and an 8x1 MUX. ALU operations and instruction required operation is given following tables.


alu_ctr	Operation
000	ADD
001	SUB
010	MULT
011	AND
100	OR
101	SLT
110	SRL
111	SLL

instruction	ALU Operation
add	ADD
sub	SUB
addi	ADD
li	X
lw	ADD
SW	ADD
beq	ADD
bne	SUB
slt	SUB
slti	SUB
j	X
jr	X
jal	X
and	AND
or	OR
andi	AND
ori	OR
sll	SLL
srl	SRL

#### 5. mult\_16

 


 A sequential 16-bit multiplier which consists of control part and datapath part. Control part is basically a FSM and produce signals for the datapath part. According to control signals the multiplication performed and the result become ready after 16 clock cycle.




#### 6. Testbench and Results


mif files for memory initialization

 


Module: mips\_single\_cycle\_16

 


add \$r1, \$r2, \$r3

 


and \$r1, \$r4, \$r5

 


sub \$r1, \$r2, \$3

 


or \$r1, \$r4, \$r5

 


addi \$r1, \$r2, 15

 


slti \$r1, \$r6, 26

 


andi \$r1, \$r5, 1023

 


li \$r2, 100

 

lw \$r1, \$r0, 4 (there is a problem)

 


ori \$r5, \$r1, 0

 

 
## Module: alu\_16


Testbench results are as expected and given below. Result of ADD, SUB and MULT operations are displayed in decimal radix and the remaining operations are displayed in binary radix for better visualization.



 
## Module: mult\_16

Since this is a 16bit sequential multiplier the result found after 16 CPU cycle.



 

#### Module: instr\_mem

 

# Module: register\_file

